


# Problem Set 1: Due Tuesday 28 Jan

Physics 251


Spring 2025

These problems are designed to give you practice with Ohm's Law and basic circuits.

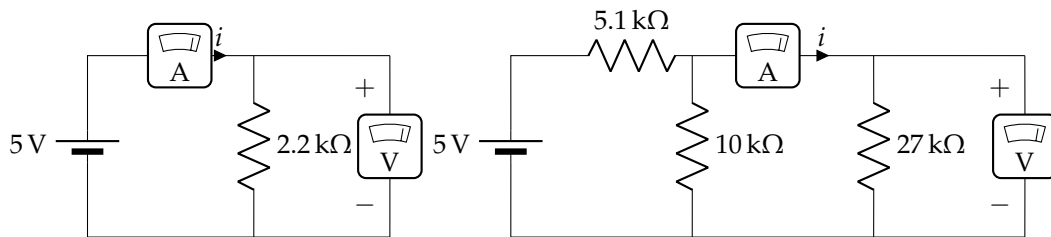
- Find the voltmeter and ammeter readings in the two circuits below. Briefly explain your thinking and show any needed calculations neatly and box your answers.



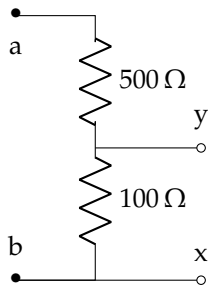
- An ideal voltage source which supplies 12 Volts DC is connected between the points marked  $a$  and  $b$  in the circuits below. Point  $a$  is positive relative to point  $b$ . Find the voltage between the points marked  $x$  and  $y$  and note whether  $x$  or  $y$  is at a higher potential.




(a)

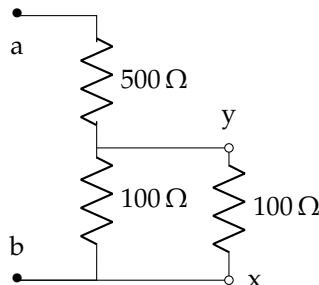


(b)

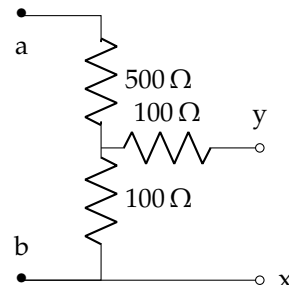


(c)

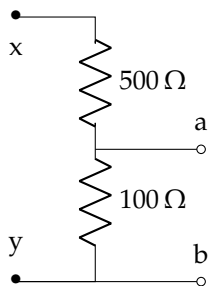

(d)

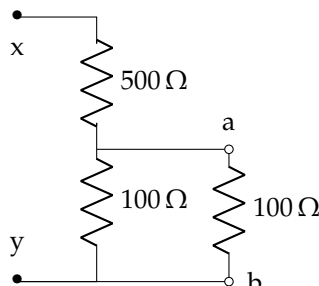

(e)

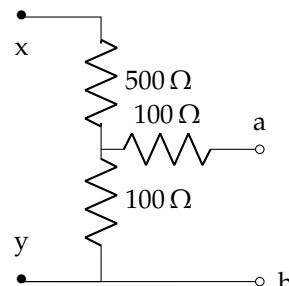

(f)

3. Repeat problem 2; only this time assume an ideal current source of 20 mA is connected between  $a$  and  $b$ . The current flows into  $a$ .
4. A large number of high precision  $10\ \Omega$  resistors is available. Find a way to produce each of the following values of resistance:
  - a)  $5\ \Omega$
  - b)  $30\ \Omega$
  - c)  $25\ \Omega$
  - d)  $9\ \Omega$
  - e)  $\frac{\pi^2}{6}\ \Omega$